

# RISC-V TALENT DEVELOPMENT PROGRAM - 2025

Powered by Samsung Semiconductor India Research(SSIR) along with VLSI System  
Design(VSD)

TITLE OF PROJECT : Digital Lock System

Submitted by,

R Prajwal

3<sup>rd</sup> Year ECE

THE NATIONAL INSTITUTE OF ENGINEERING MYSURU

**Course Instructor**

Kunal Ghosh

CO-FOUNDER OF VLSI SYSTEM DESIGN(VSD)

## Contents

1.	Overview
2.	Components Required
3.	Pinout Diagram
4.	Table of Pin Connection

# 1.Overview

The **Digital Lock System** is an embedded security project that uses a 4-bit password to control access. The system:

- Takes password input from 4 push buttons.
- Verifies the entered password against a predefined password (1010).
- Unlocks (Green LED ON) if the password is correct.
- Locks (Red LED ON) if the password is incorrect.
- Locks permanently after **three failed attempts** (requires reset to unlock).

User enters a 4-bit password using push buttons.

Press the "Enter" button to submit the password.


The system compares the input with the stored password.

If correct → Green LED turns ON, Red LED remains OFF, If incorrect → Red LED turns ON, After 3 incorrect attempts, the system locks permanently, To reset the system, use the built-in reset button on the VSDSquadron Mini board.

## 2.Components Required to build Smart Door:

- VSDSquadron Mini Board
- 4 Push Buttons (PD1-PD4) – Used for entering the 4-bit password.
- 1 Enter Button (PD5)
- 2 LEDs (PC6, PC7)
- Green LED (PC6) → Unlock indicator
- Red LED (PC7) → Lock indicator

## 3. Pinout Diagram

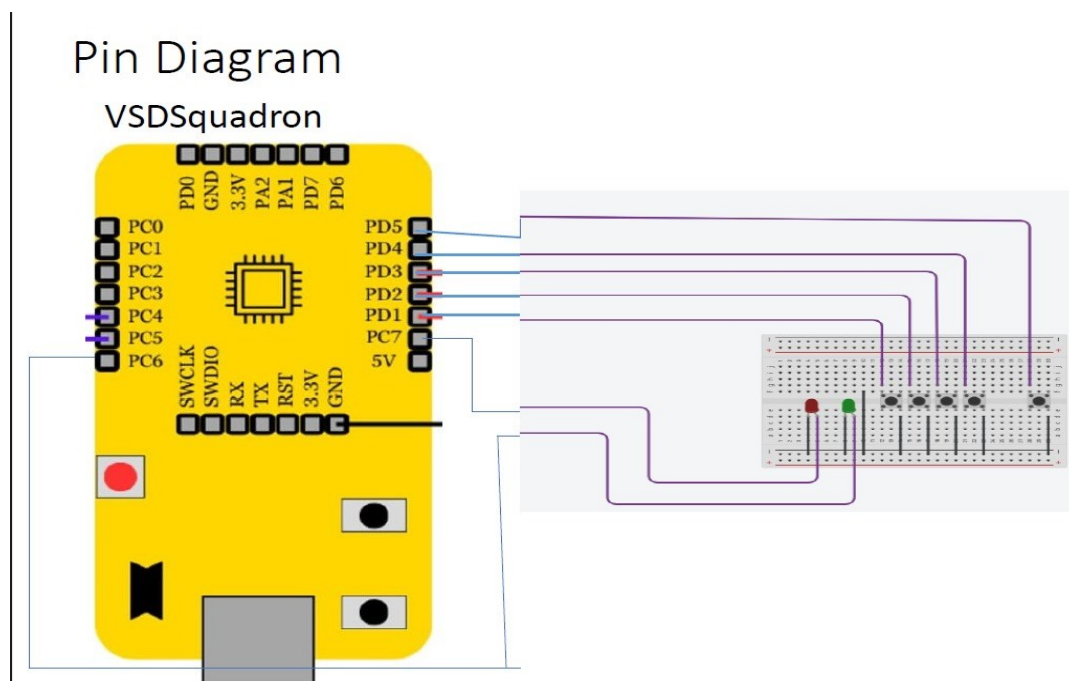

## 4. Table of Pin Connection

VSDSquadron mini board   Hardware Connections	
GND	Led cathode, <a href="#">Switch</a> (1,2,3,4,5) cathode
PD1	Switch 1 anode
PD2	Switch 2 anode
PD3	Switch 3 anode
PD4	Switch 4 anode
PD5	Submit password
<a href="#">Pull-up-Resistor</a>	10kohm
PC7	Red led (LOCKED)
PC6	Green <a href="#">Led</a> (Unlocked)